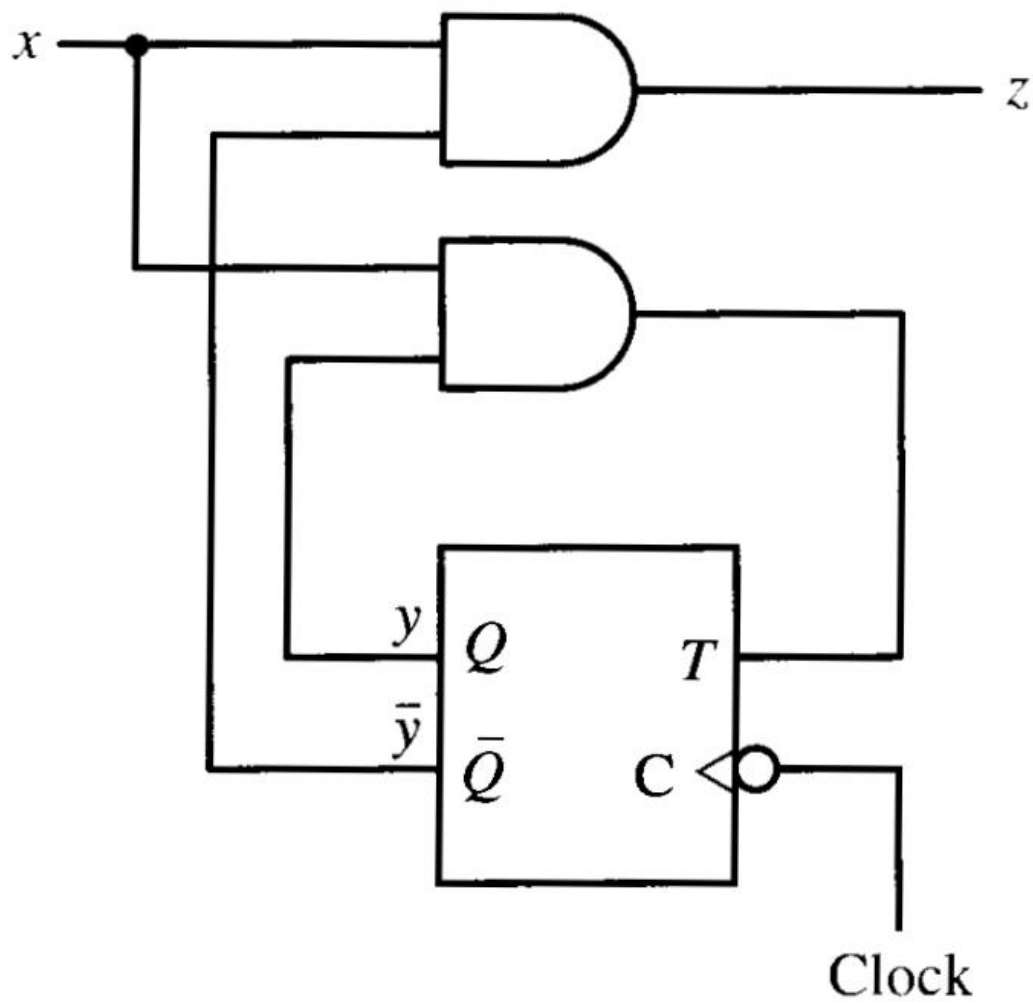


For the synchronous sequential circuit of the figure, find:

(a) The state table. Assign $A = 0$, $B = 1$.

(b) The state diagram.

(c) The timing diagram for an input sequence $x = 00100110$ and the starting state $y^0 = 1$.




- Given the synchronous sequential circuit of the figure with level inputs:

(a) Draw a timing diagram for $x = 000101011$ and the initial state of the flip flop is equal to 0 ($y^0 = 0$).

(b) Find the state diagram.

(c) Find the state table.

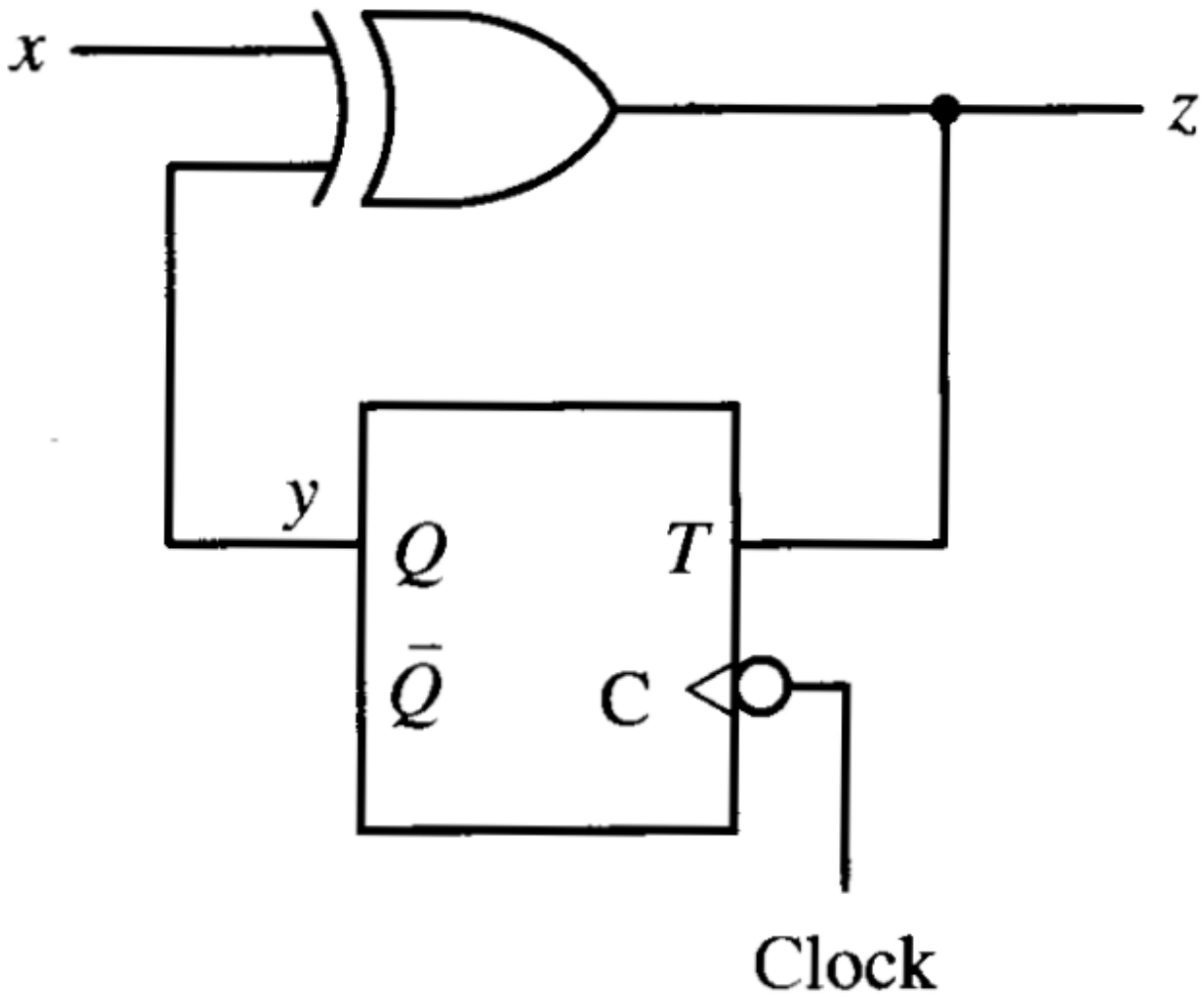

- For the sequential circuit in the figure, find:

(a) The state table ($A=0$, $B=1$).

(b) The state diagram.

(c) A timing diagram if the starting state is $y^0 = 0$ and $x = 001011000$.

This circuit is level synchronous.

